

DC & Transient Response Outline

- ☐ DC Response
- ☐ Logic Levels and Noise Margins
- ☐ Transient Response
- ☐ Delay Estimation

DC Response

❑ DC Response: V_{out} vs. V_{in} for a gate (input)

❑ Ex: Inverter


– When $V_{in} = 0$ $\rightarrow V_{out} = V_{DD}$

– When $V_{in} = V_{DD}$ $\rightarrow V_{out} = 0$

– In between, V_{out} depends on transistor size and current

– By KCL, must settle such that



$$I_{dsn} = -I_{dsp} = I_{sdp}$$

 

Operating Regions

❑ Transistor operating regions


Region	nMOS	pMOS
A	Cutoff	Linear
B	Saturation	Linear
C	Saturation	Saturation
D	Linear	Saturation
E	Linear	Cutoff

  

Operating Regions

□ Revisit transistor operating regions


Region	nMOS	pMOS
A	Cutoff	Linear
B	Saturation	Linear
C	Saturation	Saturation
D	Linear	Saturation
E	Linear	Cutoff

 

C point is called switching point, is about $V_{DD}/2$ if $\beta_n = \beta_p$


Beta Ratio

 - ❑ If $\beta_p / \beta_n \neq 1$, switching point will move from $V_{DD}/2$
- ❑ Called *skewed* gate
- ❑ Other gates: collapse into equivalent inverter




Beta Ratio

 - ❑ If $\beta_p / \beta_n \neq 1$, switching point will move from $V_{DD}/2$
- ❑ Called *skewed* gate
- ❑ Other gates: collapse into equivalent inverter




Noise Margins

 

- How much noise can a gate input see before it does not recognize the input?




Inverter buffer

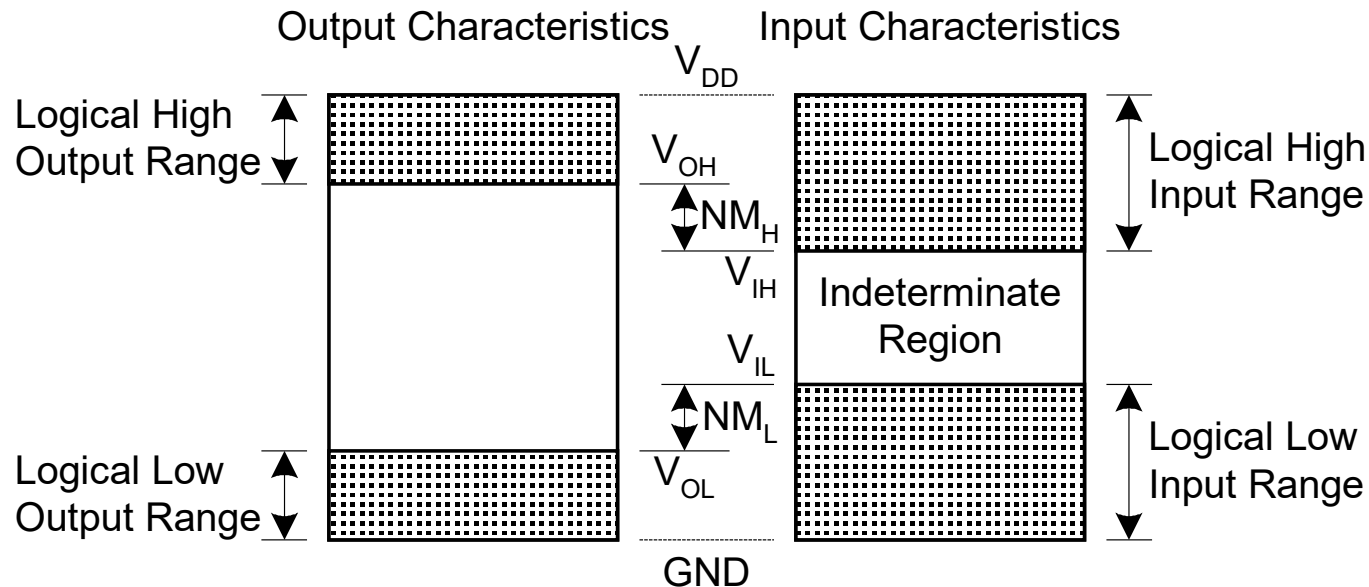


Noise Margins

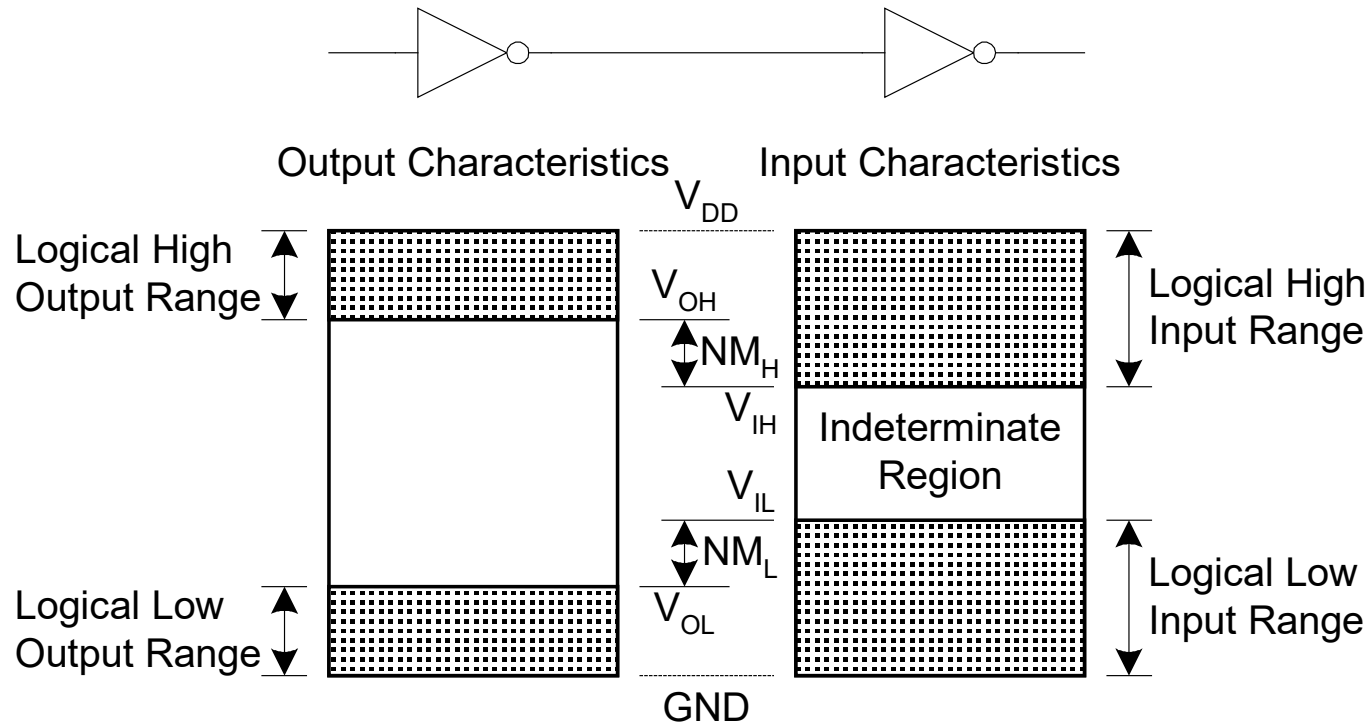- ❑ Low Noise Margin $NM_L = V_{IL} - V_{OL}$; High $NM_H = V_{OH} - V_{IH}$;
 V_{IH} =minimum high input voltage; V_{IL} =maximum low input voltage
 V_{OH} =minimum high output voltage; V_{OL} =maximum low output voltage



Logic Levels

 - ❑ To maximize noise margins, select logic levels at negative unity gain point of DC transfer characteristic



Exercise

□ 2.2, 2.4, 2.7, 2.14, 2.15, 2.16, 2.21, 2.22, 3.7

Transient Response

- ❑ *DC analysis* tells us V_{out} if V_{in} is constant regarding of time
- ❑ *Transient analysis* tells us $V_{out}(t)$ if $V_{in}(t)$ changes following time
 - Requires solving differential equations
- ❑ Input is usually considered to be a step or ramp signal
 - From 0 to V_{DD} or vice versa

Inverter Step Response



□ Ex: find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$

$$\frac{dV_{out}(t)}{dt} = -\frac{I_{dsn}(t)}{C_{load}}$$
 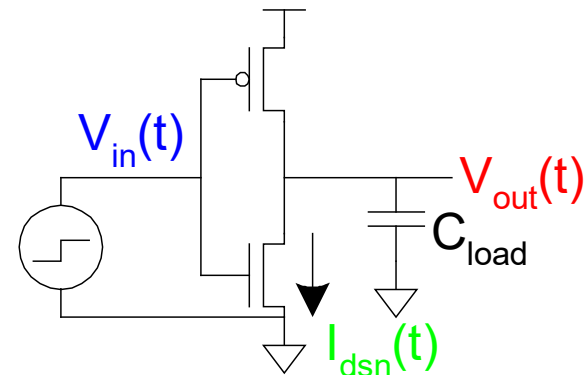
$$I_{dsn}(t) = \begin{cases} 0 & t \leq t_0 \\ \frac{\beta}{2}(V_{DD} - V_t)^2 & V_{out} > V_{DD} - V_t \\ \beta\left(V_{DD} - V_t - \frac{V_{out}(t)}{2}\right)V_{out}(t) & V_{out} < V_{DD} - V_t \end{cases}$$



Delay Types

- ❑ Delay determines how quickly the circuit is able to process data.
- ❑ In **combinational** circuit, two types of delay are important: **contamination** delay and **propagation** delay.

Propagation Delay Definition

- ❑ **Propagation** delay is the time it takes from a change in the input to the completion (switching point) of the change in the output (worst delay)
- ❑ t_{pdr} : *rising propagation delay*
 - From input change crossing $V_{DD}/2$ to **rising** output crossing $V_{DD}/2$ (upper bound)
- ❑ t_{pdf} : *falling propagation delay*
 - From input change crossing $V_{DD}/2$ to **falling** output crossing $V_{DD}/2$ (upper bound)
- ❑ t_{pd} : *average propagation delay*
 - $t_{pd} = (t_{pdr} + t_{pdf})/2$
- ❑ t_r : *rise time*
 - From output crossing 0.2 (0.1) V_{DD} to 0.8 (0.9) V_{DD}
- ❑ t_f : *fall time*
 - From output crossing 0.8 (0.9) V_{DD} to 0.2 (0.1) V_{DD}

Propagation Delay


 
 


FIG 5.7 Unloaded inverter


Delay

 

- When different logic gates are connected to form a circuit, the contamination and propagation delays of the individual gates sum to form the overall circuit delays.
- Because contamination delay refers to the **start** of the output change: Overall contamination delay for a circuit is the **smallest** sum of contamination delays through gates from input to output.
- Conversely, since propagation delay refers to the **completion** of the output change: Overall propagation delay for a circuit is the **largest** sum of propagation delays through gates from input to output.

Simulated Inverter Delay

 - ❑ Solving differential equations by hand is too hard
- ❑ SPICE simulator solves the equations numerically
 - Uses more accurate I-V models too!
- ❑ But simulations do take time to complete for large circuits



Delay Estimation

- ❑ We would like to be able to easily estimate delay
 - Not as accurate as simulation
 - But easier to ask “What if?”
- ❑ The step response usually looks like a 1st order RC response with a decaying exponential.
- ❑ Use RC delay models to estimate delay
 - C = total capacitance on **output node**
 - Use *effective resistance* R
 - So that $t_{pd} = RC$
- ❑ Characterize transistors by finding their effective R
 - Depends on average current as gate switches

RC Values

❑ Capacitance

- $C = C_g = C_{sb} = C_{db} = 2 \text{ fF}/\mu\text{m}$ of gate width
- Values similar across many processes

❑ Resistance



- $R \approx 2 \text{ K}\Omega \cdot \mu\text{m}$ in 180 nm process
- Improves with shorter channel lengths

❑ Unit transistors

- May refer to minimum contacted device ($4\lambda/2\lambda$)
- Or maybe $1 \mu\text{m}$ wide device
- Doesn't matter as long as you are consistent


RC Delay Model

  - ❑ Use equivalent circuits for MOS transistors
 - Ideal switch + capacitance and **ON** resistance
 - Unit nMOS has resistance R , capacitance C
 - Unit pMOS has resistance $2R$, capacitance C
- ❑ Capacitance **proportional to width**
- ❑ Resistance **inversely proportional** to width



Inverter Delay Estimate

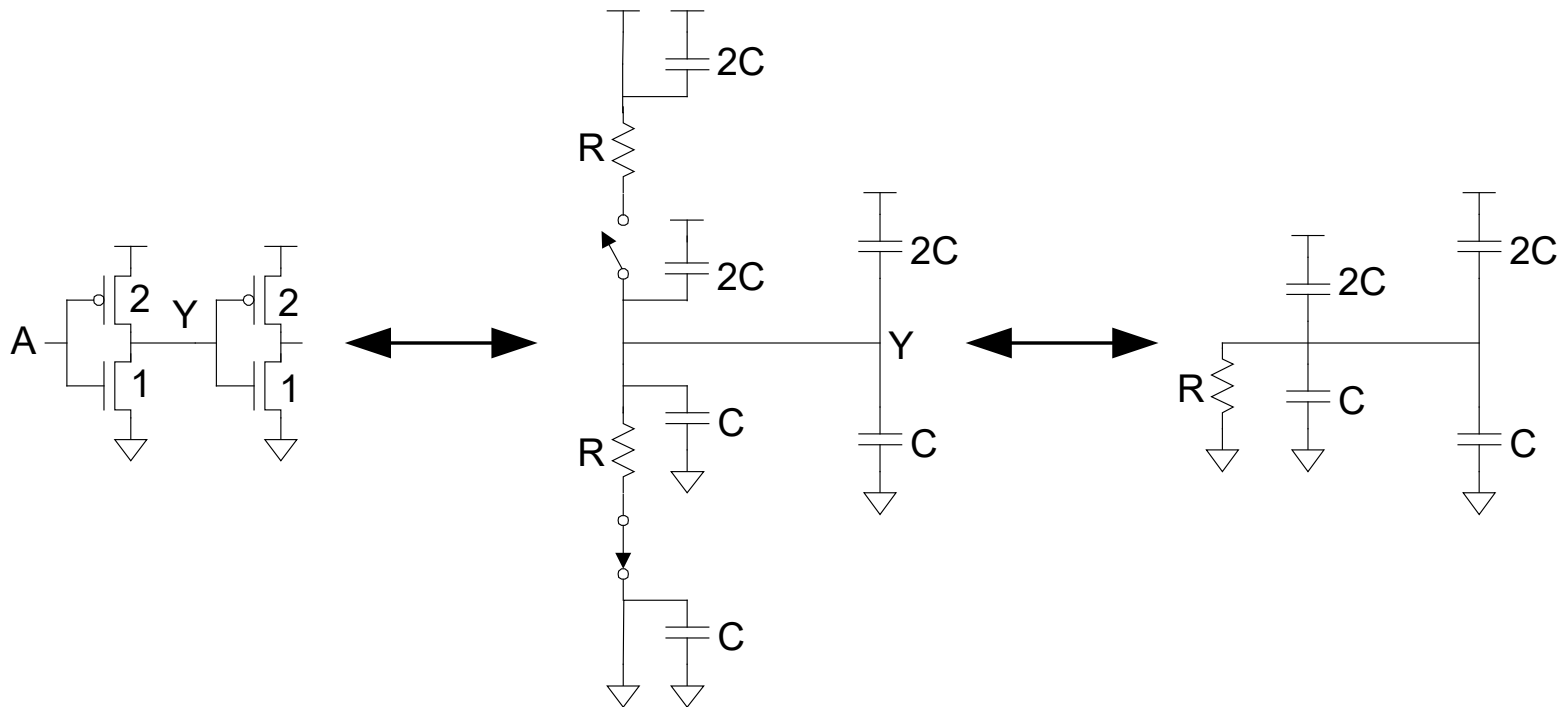
- Estimate the delay of a fanout-of-1 inverter at node Y



$$d = 6RC$$

 
Example: 3-input NAND sizes

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).



 
Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).





3-input NAND Caps

 - ❑ Annotate the 3-input NAND gate with gate and diffusion capacitance.



3-input NAND Caps

 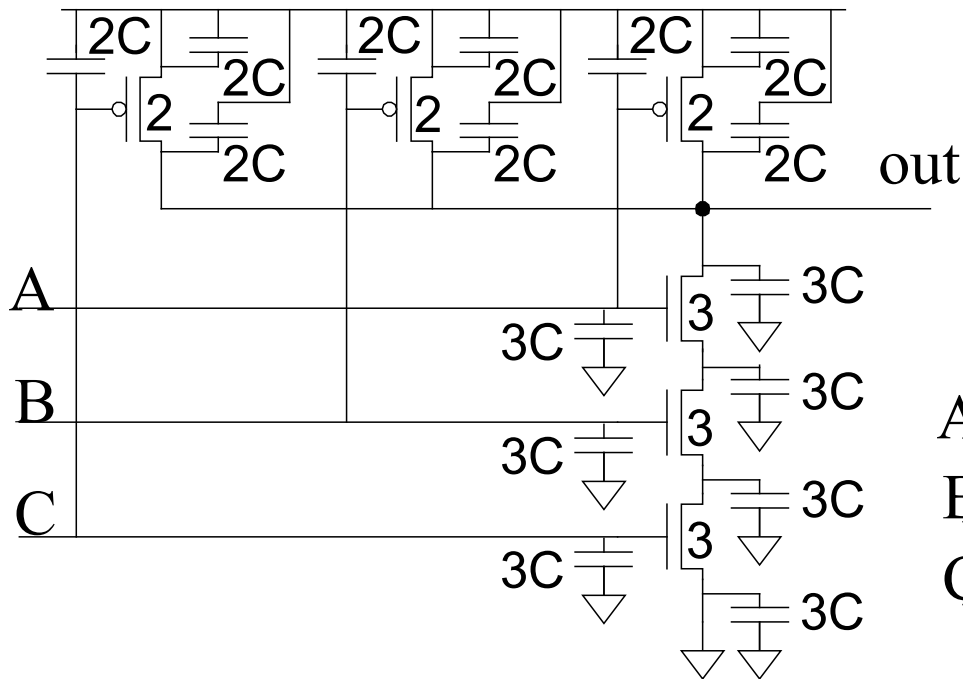- Annotate the 3-input NAND gate with gate and diffusion capacitance.




Elmore Delay

- ❑ ON transistors look like resistors
- ❑ Pullup or pulldown network modeled as *RC ladder*
- ❑ Elmore delay of RC ladder


$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$
 
$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$



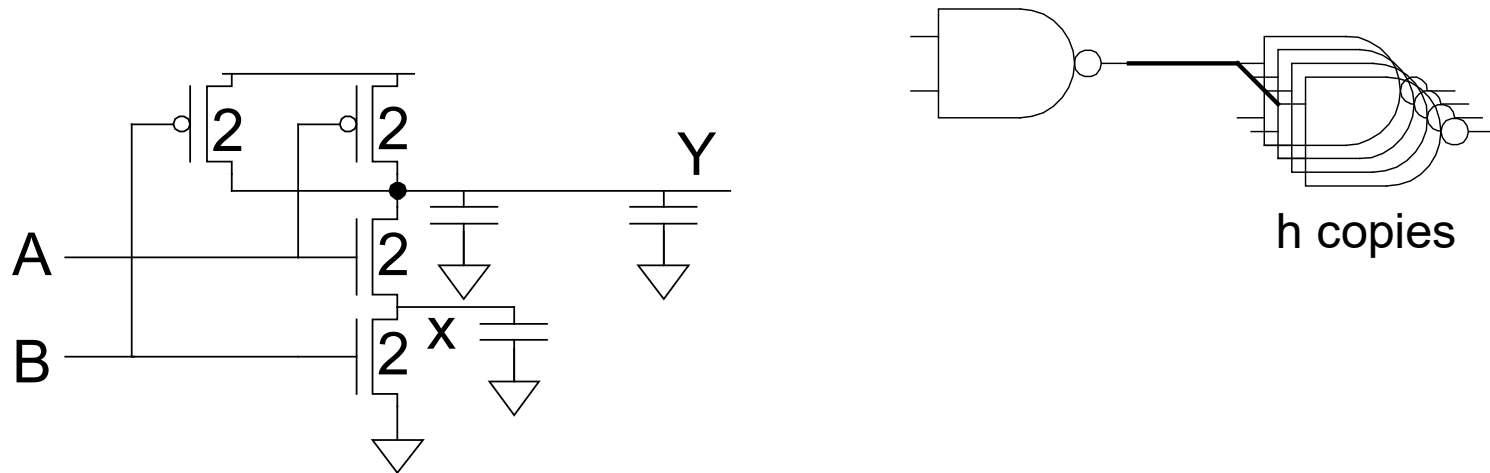
Example: 2-input NAND

- Estimate worst-case rising and falling delay of 2-input NAND driving h identical gates.




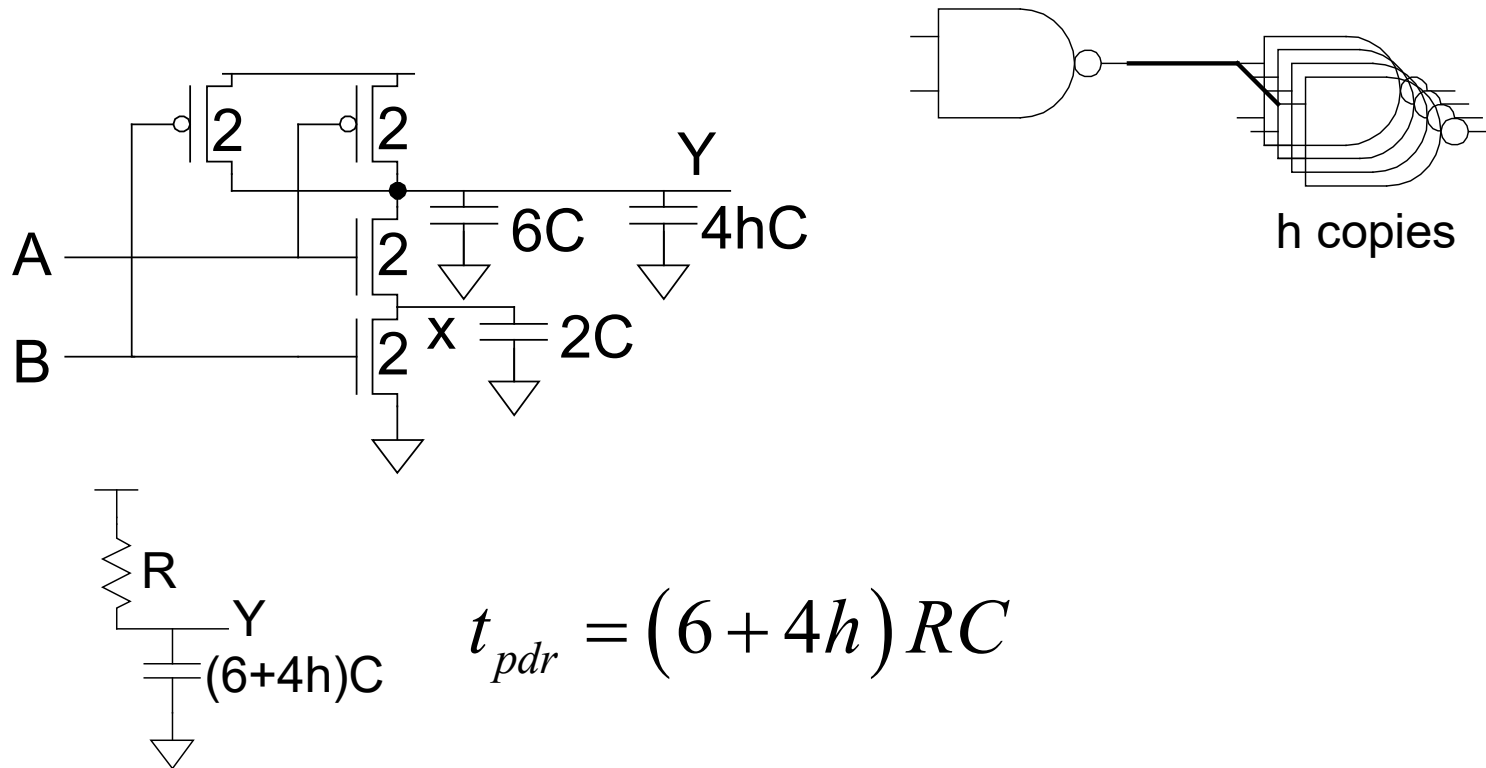
Example: 2-input NAND

- Estimate worst case **rising** propagation delays of a 2-input NAND driving h identical gates.



 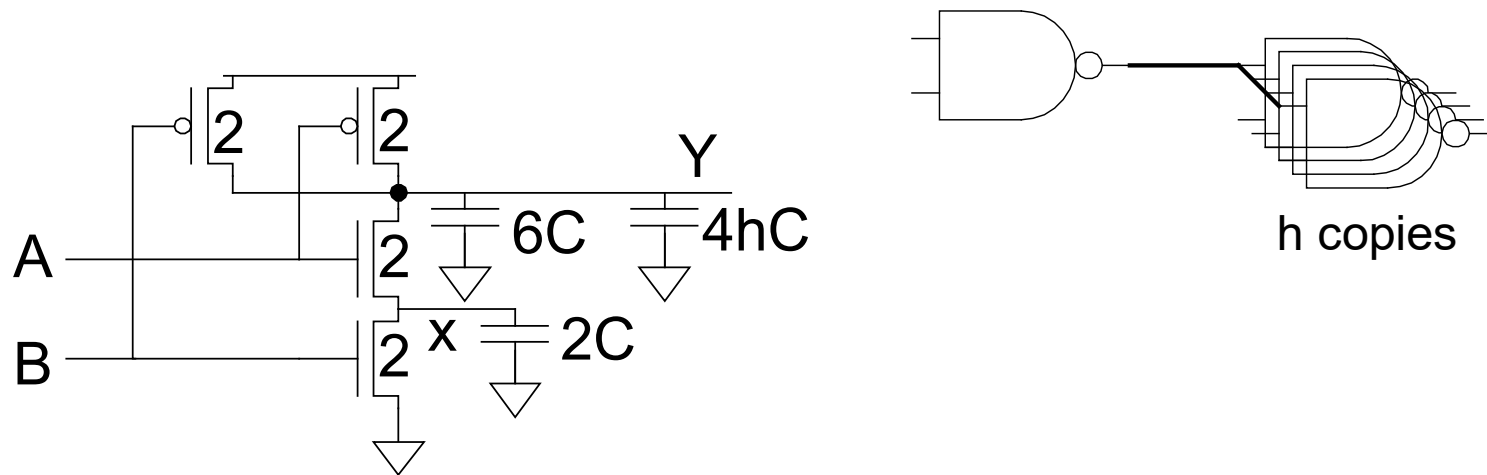Example: 2-input NAND

- Estimate **falling** propagation delays of a 2-input NAND driving h identical gates.



$$t_{pdf} = (2C)\left(\frac{R}{2}\right) + \left[(6 + 4h)C\right]\left(\frac{R}{2} + \frac{R}{2}\right)$$


$$= (7 + 4h)RC$$

Delay Components

- Delay has two parts (components)
 - *Parasitic delay*—determined by the gate driving its **own internal** diffusion capacitance
 - 6 RC or 7 RC for the previous NAND2
 - Independent of load
 - *Effort delay*—depends on the ratio of external load capacitance to input capacitance. The capacitance ratio is called the **electrical effort** or **fanout**, will be discussed later.
 - 4h RC for the previous NAND2
 - Proportional to load capacitance

Contamination Delay

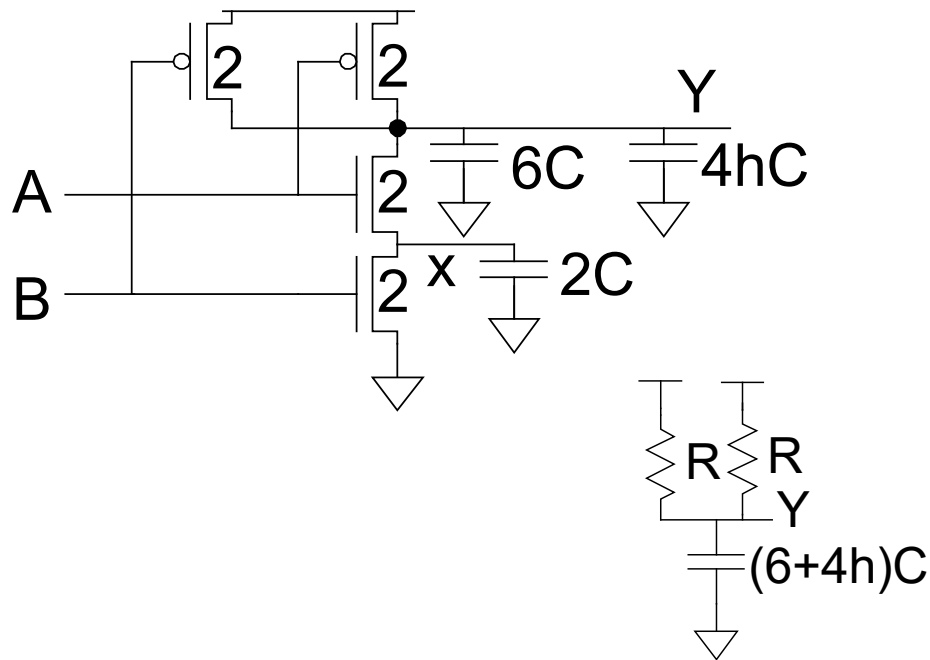
- ❑ Best-case (contamination) delay can be substantially less than propagation delay.
- ❑ Ex: If both inputs fall (from '1' go to '0') simultaneously



$$t_{cdr} = (3 + 2h)RC$$



Diffusion Capacitance

 - ❑ we assumed contacted diffusion on every s and d.
- ❑ *Good layout minimizes* diffusion area
- ❑ Ex: NAND3 layout shares one diffusion contact
 - Reduces output capacitance by 2C
 - Merged uncontacted diffusion help too



Layout Comparison

❑ Which layout is better?

  

Exercise

- ❑ 4.2, 4.3, 4.4
- ❑ Develop an one bit full adder function and schematic circuit
- ❑ Develop a half adder function and schematic circuit
- ❑ Draw the schematic circuits of a latch and a rising edge trigger DFF (refer to the previous class note by using transmission gate and other logic)