

# Wire Outline


---

- ☐ Introduction
- ☐ Interconnect Modeling
  - Wire Resistance
  - Wire Capacitance
- ☐ Wire RC Delay
- ☐ Crosstalk
- ☐ Wire Engineering
- ☐ Repeaters

# Introduction


- ❑ Chips are mostly made of wires called *interconnect*
  - In stick diagram, wires set size
  - Transistors are little things under the wires
  - Many layers of wires
- ❑ Wires are as important as transistors
  - Speed
  - Power
  - Noise
- ❑ Alternating layers run orthogonally
 
# Layout of Two Stage Pipelined Delta Sigma ADC




ADC

# Example

 

Intel 90 nm Stack

[Thompson02]

 


Intel 45 nm Stack

[Moon08]
 
# Wire Geometry

- ❑ Pitch =  $w + s$
- ❑ Aspect Ratio:  $AR = t/w$ 
  - Old processes had  $AR \ll 1$
  - Modern processes have  $AR \approx 2$ 
    - Pack in many skinny wires




# Layer Stack

- ❑ AMI (On) Semiconductor 0.6  $\mu\text{m}$  process has 3 metal layers
  - M1 for within-cell routing
  - M2 for vertical routing between cells
  - M3 for horizontal routing between cells
- ❑ Modern processes use 6-10+ metal layers
  - M1: thin, narrow ( $< 3\lambda$ )
    - High density cells
  - Mid layers
    - Thicker and wider, (density vs. speed)
  - Top layers: thickest
    - For  $V_{DD}$ , GND, clk

 
# Lumped Element Models

- ❑ Wires are a distributed system
  - Approximate with lumped element models



- ❑ 3-segment  $\pi$ -model is accurate to 3% in simulation
- ❑ L-model needs 100 segments for same accuracy!
- ❑ T model is harder to be solved
- ❑ Use **single segment  $\pi$ -model** for Elmore delay

# Multi-segment Models

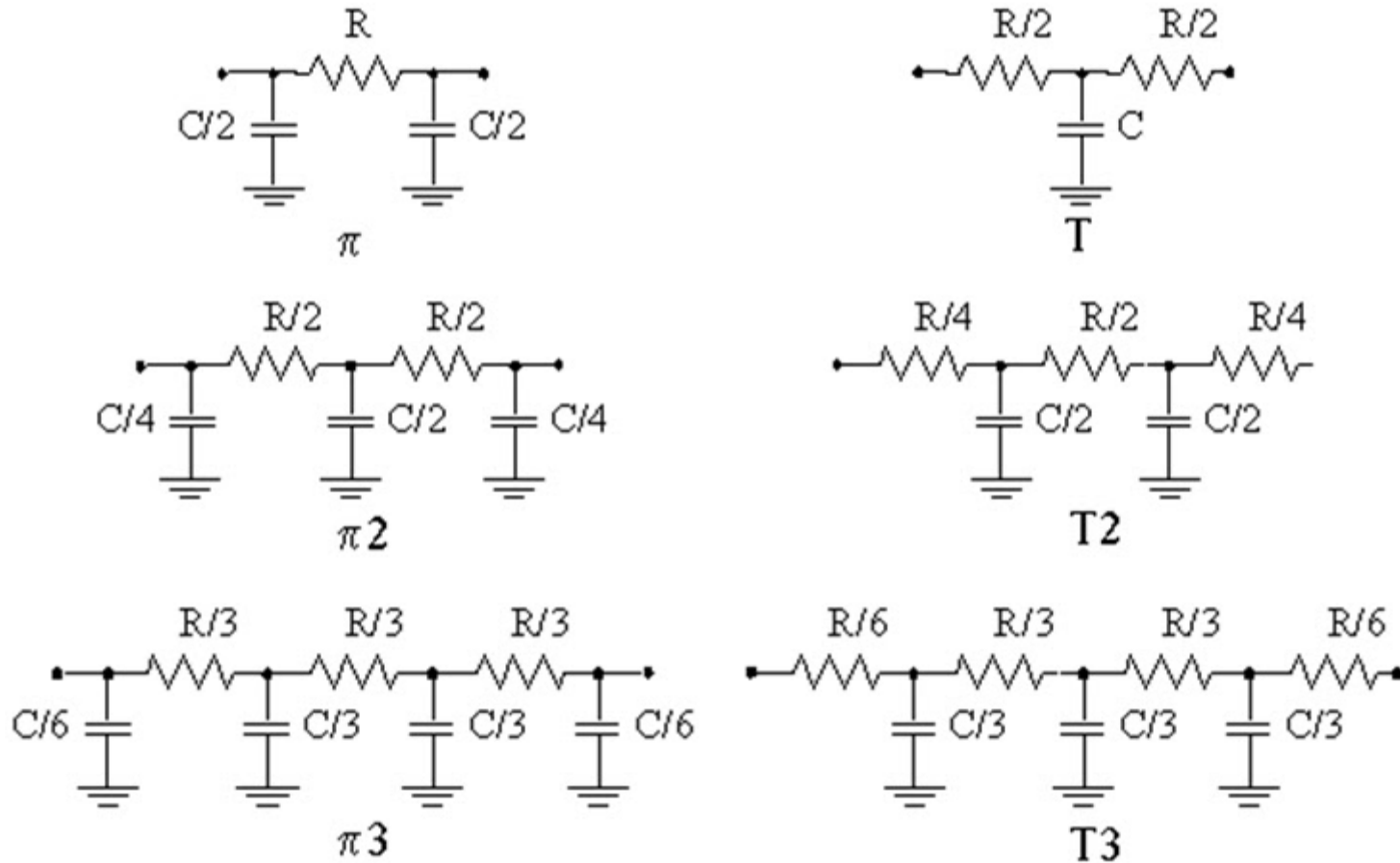




# Wire Resistance

□  $\rho = \text{resistivity } (\Omega \cdot \text{m})$

$$R = \frac{\rho}{t} \frac{l}{w} = R_{\square} \frac{l}{w}$$

□  $R_{\square} = \text{sheet resistance } (\Omega/\square)$   
 – □ is a **dimensionless unit**(!)

 □ Count number of squares  
 –  $R = R_{\square} * (\# \text{ of squares})$



# Choice of Metals

- ❑ Until 180 nm generation, most wires were aluminum
- ❑ Contemporary processes normally use copper
  - Cu atoms diffuse into silicon and damage FETs
  - Must be surrounded by a diffusion barrier

Metal	Bulk resistivity $\rho$ ( $\mu\Omega \cdot \text{cm}$ )
Silver (Ag)	1.6
Copper (Cu)	1.7
Gold (Au)	2.2
Aluminum (Al)	2.8
Tungsten (W)	5.3
Titanium (Ti)	43.0

# Typical Sheet Resistance

- Sheet resistance for 180nm process with Aluminum interconnect

Table 4.7 Sheet resistances	
Layer	Sheet Resistance ( $\Omega / \square$ )
Diffusion (silicided)	3-10
Diffusion (unsilicided)	50-200
Polysilicon (silicided)	3-10
Polysilicon (unsilicided)	50-400
Metal1	0.08
Metal2	0.05
Metal3	0.05
Metal4	0.03
Metal5	0.02
Metal6	0.02

# Contacts Resistance


- ❑ Contacts and vias also have 2-20  $\Omega$
- ❑ Use many contacts for lower R
  - Many small contacts for current crowding around periphery


 
# Copper Issues

- ❑ Copper wires diffusion barrier has high resistance
- ❑ Copper is also prone to *dishing* during polishing
- ❑ Effective resistance is higher

$$R = \frac{\rho}{(t - t_{\text{dish}} - t_{\text{barrier}})} \frac{l}{(w - 2t_{\text{barrier}})}$$



## Example

- ❑ Compute the sheet resistance of a  $0.17\text{ }\mu\text{m}$  thick Cu wire in a 65 nm process. Ignore dishing.

$$R_{\square} = .$$

- ❑ Find the total resistance if the wire is  $0.125\text{ }\mu\text{m}$  wide and 1 mm long. Ignore the barrier layer.

$$R =$$

## Example

- ❑ Compute the sheet resistance of a 0.17  $\mu\text{m}$  thick Cu wire in a 65 nm process. Ignore dishing.


$$R_{\square} = \frac{1.7 \times 10^{-8} \Omega\text{m}}{.17 \times 10^{-6} \text{ m}} = 0.10 \Omega/\square$$

- ❑ Find the total resistance if the wire is 0.125  $\mu\text{m}$  wide and 1 mm long. Ignore the barrier layer.

$$R = (0.10 \Omega/\square) \frac{1000 \mu\text{m}}{0.125 \mu\text{m}} = 800 \Omega$$
 
# Wire Capacitance

- ❑ Wire has capacitance per unit length
  - To neighbors
  - To layers above and below
- ❑  $C_{\text{total}} = C_{\text{top}} + C_{\text{bot}} + 2C_{\text{adj}}$





# Capacitance Trends

- ❑ Parallel plate equation:  $C = \epsilon_{ox} A/d$ 
  - Wires are not parallel plates, but obey trends
  - Increasing area (W, t, L) increases capacitance
  - Increasing distance (s, h) decreases capacitance
- ❑ Dielectric constant (permittivity)
  - $\epsilon_{ox} = k\epsilon_0$ 
    - $\epsilon_0 = 8.85 \times 10^{-14}$  F/cm
    - $k = 3.9$  for  $\text{SiO}_2$
- ❑ Processes are starting to use low-k dielectrics
  - $k \approx 3$  (or less) as dielectrics use air pockets

# Capacitance Formula

- ❑ Capacitance of a line without neighbors can be approximated as

$$C_{tot} = \epsilon_{ox} l \left[ \frac{w}{h} + 0.77 + 1.06 \left( \frac{w}{h} \right)^{0.25} + 1.06 \left( \frac{t}{h} \right)^{0.5} \right] \approx l * C / \mu m$$

- ❑ This empirical formula is accurate to 6% for AR < 3.3


# Diffusion & Polysilicon

- ❑ Diffusion capacitance is very high (1-2 fF/μm)
  - Comparable to gate capacitance
  - Diffusion also has high resistance
  - Avoid using **diffusion runners** for wires!
- ❑ Polysilicon has lower C but high R
  - Use for **transistor gates**
  - Occasionally for very short wires between gates

# Wire RC Delay


- Estimate the delay of a 30 units inverter driving a 6 units inverter at the end of the 1 mm copper wire (0.17 $\mu$ m thickness and 0.125 $\mu$ m width). Assume wire capacitance is 0.2 fF/ $\mu$ m and that a unit-sized inverter has  $R = 10\text{ K}\Omega$  for nMOS and  $C = 1.0\text{ fF}$ .

–  $t_{pd} =$

 
 
# Wire RC Delay

- ❑ Estimate the delay of a 30 units inverter driving a 6 units inverter at the end of the 1 mm copper wire (0.17 $\mu$ m thickness and 0.125 $\mu$ m width). Assume wire capacitance is 0.2 fF/ $\mu$ m and that a unit-sized inverter has  $R = 10\text{ K}\Omega$  for nMOS and  $C = 1.0\text{ fF}$ .
  - $t_{pd} = (1000\ \Omega)(130\text{ fF}) + (1000 + 800)\ \Omega (100 + 6)\text{ fF} = 320.8\text{ ps}$





# Wire Energy

- ❑ Estimate the energy per unit length (mm) to send a bit of information (one rising and one falling transition) in a CMOS process (65 nm,  $V_{dd}=1.0\text{v}$ ).

- ❑  $E = CV^2$   
 $= (0.2 \text{ pF/mm})(1.0 \text{ V})^2$   
 $= 0.2 \text{ pJ/bit/mm}$   
 $= 0.2 \text{ mW}/(\text{Gb/s})/\text{mm}$
  
# Repeaters

- ❑ R and C are proportional to  $L$
- ❑ RC delay is proportional to  $L^2$ 
  - Unacceptably great for long wires
- ❑ Break long wires into  $N$  shorter segments
  - Drive each one with an inverter or buffer



# Repeater Design

- ❑ How many repeaters should we use?
- ❑ How large should each one be?
- ❑ Equivalent Circuit-- Wire has resistance  $R_w$  and  $C_w$  per unit length
  - Single wire segment--wire length =  $L/N$ 
    - Wire Capacitance  $C_w * L/N$ , Resistance  $R_w * L/N$
  - Inverter width  $3W$  (nMOS =  $W$ , pMOS =  $2W$ )
    - Gate Capacitance  $C' * W$ , Resistance  $R/W$ ,  $C' = 3C_{\text{unit}}$



# Repeater Results

## □ Write equation for Elmore Delay

The Elmore delay of each segment is

$$t_{pd-seg} = \frac{R}{W} \left( \frac{C_w l}{N} + C' W \right) + \left( \frac{R_w l}{N} \right) \left( \frac{C_w l}{2N} + C' W \right)$$

The total delay is  $N$  times greater:

$$t_{pd} = NRC' + L \left( R_w C' W + \frac{RC_w}{W} \right) + L^2 \frac{R_w C_w}{2N}$$

Take the partial derivatives with respect to  $N$  and  $W$  and set them to 0 to minimize delay:

$$\begin{aligned} \frac{\partial t_{pd}}{\partial N} &= RC' - l^2 \frac{R_w C_w}{2N^2} = 0 \Rightarrow N = l \sqrt{\frac{R_w C_w}{2RC'}} \\ \frac{\partial t_{pd}}{\partial W} &= l \left( R_w C' - \frac{RC_w}{W^2} \right) = 0 \Rightarrow W = \sqrt{\frac{RC_w}{R_w C'}} \end{aligned}$$

# Repeater Results

## □ Summary

The best length of wire between repeaters is  $\frac{l}{N} = \sqrt{\frac{2RC'}{R_w C_w}}$   
The best number of segment, **N=?**

The delay per unit length is

$$\frac{t_{pd}}{l} = (2 + \sqrt{2}) \sqrt{RC'R_w C_w} \quad \begin{array}{l} \sim 40 \text{ ps/mm} \\ \text{in 65 nm process} \end{array}$$

**The total delay of the entire length is ?**

The inverter nMOS transistor width is  $W = \sqrt{\frac{RC_w}{R_w C'}}$

# Repeater Example(1)

- Determine the best distance between repeaters for a minimum pitch **metal2** line in a 180 nm process for least delay. Assume the unit transistor resistance is  $3 \text{ k}\Omega \cdot \mu\text{m}$ , the gate unit capacitance is  $C=1.7 \text{ fF}/\mu\text{m}$ , and the **metal2** per unit length capacitance is  $C_w=0.21 \text{ fF}/\mu\text{m}$ , resistance is  $R_w=0.16 \Omega / \mu\text{m}$ .

1) How far should the repeater be spaced?

$$\text{repeaters spaced} = \frac{l}{N} = \sqrt{\frac{2RC'}{R_w C_w}} = \sqrt{\frac{2(3000\Omega \cdot \mu\text{m})\left(5.1 \frac{\text{fF}}{\mu\text{m}}\right)}{\left(0.16 \frac{\Omega}{\mu\text{m}}\right)\left(0.21 \frac{\text{fF}}{\mu\text{m}}\right)}} = 950 \mu\text{m}$$

$$C'=3C= 5.1 \text{ fF}/\mu\text{m}$$

# Repeater Example(2)

- Determine the best distance between repeaters for a minimum pitch **metal2** line in a 180 nm process. Assume the unit transistor resistance is  $3 \text{ k}\Omega \cdot \mu\text{m}$ , the gate unit capacitance is  $C = 1.7 \text{ fF}/\mu\text{m}$ , and the **metal2** per unit length capacitance is  $C_w = 0.21 \text{ fF}/\mu\text{m}$ , resistance is  $R_w = 0.16 \Omega / \mu\text{m}$ .
  - 1) How far should the repeater be spaced?
  - 2) How wide should the repeater transistor be?

$$W = \sqrt{\frac{RC_w}{R_w C'}} = \sqrt{\frac{(3000 \Omega \cdot \mu\text{m}) \left( 0.21 \frac{\text{fF}}{\mu\text{m}} \right)}{\left( 0.16 \frac{\Omega}{\mu\text{m}} \right) \left( 5.1 \frac{\text{fF}}{\mu\text{m}} \right)}} = 28 \mu\text{m} = W_n, W_p \approx 2W_n$$

# Repeater Example(3)

- Determine the best distance between repeaters for a minimum pitch **metal2** line in a 180 nm process. Assume the unit transistor resistance is  $3 \text{ k}\Omega \cdot \mu\text{m}$ , the gate unit capacitance is  $C_g = 1.7 \text{ fF}/\mu\text{m}$ , and the **metal2** per unit length capacitance is  $C_w = 0.21 \text{ fF}/\mu\text{m}$ , resistance is  $R_w = 0.16 \Omega / \mu\text{m}$ .

3) What is the delay per unit length (**mm**) of the wire

delay per unit length

$$\begin{aligned} &= (2 + \sqrt{2}) \sqrt{RC' R_w C_w} \\ &= (2 + \sqrt{2}) \sqrt{(3000 \Omega \cdot \mu\text{m}) \left( 5.1 \frac{\text{fF}}{\mu\text{m}} \right) \left( 0.16 \frac{\Omega}{\mu\text{m}} \right) \left( 0.21 \frac{\text{fF}}{\mu\text{m}} \right)} \\ &= 77 \frac{\text{ps}}{\text{mm}} \end{aligned}$$

# Repeater Example(4)

- ❑ Determine the best distance between repeaters for a minimum pitch **metal5** line in a 180 nm process. Assume the transistor resistance is  $3 \text{ k}\Omega\cdot\mu\text{m}$ , the gate capacitance is  $C=1.7 \text{ fF}/\mu\text{m}$ , and the **metal5** capacitance is  $C_w=0.24 \text{ fF}/\mu\text{m}$ , resistance is  $R_w=0.025 \Omega/\mu\text{m}$ .
  - 1) How far should the repeater be spaced? (**2260  $\mu\text{m}$** )
  - 2) How wide should the repeater transistor be? ( **$W = 75\mu\text{m}$** )
  - 3) What is the signal delay per unit length of the wire? (**30 ps/mm**)

Summary: wide upper level metal lines are faster, but take more space. Therefore, they are precious routing resource

# Repeater Energy

- ❑ Energy / length  $\approx 1.87C_w V_{DD}^2$ 
  - 87% premium over unpeated wires
  - The extra power is consumed in the large repeaters
- ❑ If the repeaters are downsized for minimum EDP:
  - Energy premium is only 30%
  - Delay increases by 14% from min delay


# Crosstalk

- ❑ A capacitor does not like to change its voltage instantaneously.
- ❑ A wire has high capacitance to its neighbor.
  - When the neighbor switches from 1- $\rightarrow$  0 or 0- $\rightarrow$ 1, the wire tends to switch too.
  - Called capacitive *coupling* or *crosstalk*.
- ❑ Crosstalk effects
  - Noise on nonswitching wires
  - Increased delay on switching wires


 
# Crosstalk Delay

- ❑ Assume layers above and below on average are quiet
  - Second terminal of capacitor can be ignored
  - Model as  $C_{\text{gnd}} = C_{\text{top}} + C_{\text{bot}}$
- ❑ Effective  $C_{\text{adj}}$  depends on behavior of neighbors
  - *Miller effect*
  - *MCF—Miller Coupling Factor*




B	$\Delta V$	$C_{\text{eff(A)}}$	MCF
Constant	$V_{\text{DD}}$	$C_{\text{gnd}} + C_{\text{adj}}$	1
Switching with A	0	$C_{\text{gnd}}$	0
Switching opposite A	$2V_{\text{DD}}$	$C_{\text{gnd}} + 2 C_{\text{adj}}$	2
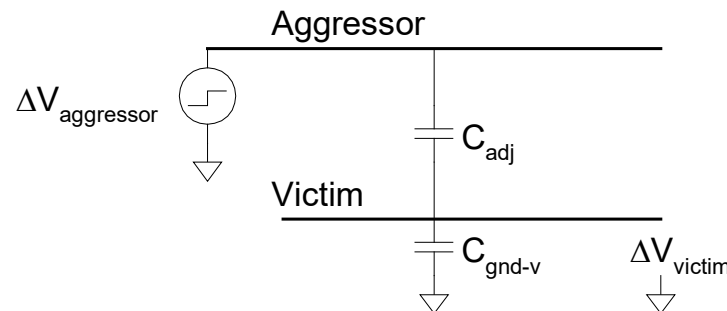
# Crosstalk Noise

- ❑ Crosstalk causes noise on nonswitching wires
- ❑ If victim is floating:
  - model as capacitive voltage divider

$$\Delta V_{victim} = \frac{C_{adj}}{C_{gnd-v} + C_{adj}} \Delta V_{aggressor}$$




# Driven Victims

- ❑ Usually victim is driven by a gate that fights noise
  - Noise depends on relative resistances
  - Victim driver is in linear region, aggressor in saturation
  - If sizes are same,  $R_{\text{aggressor}} = 2-4 \times R_{\text{victim}}$


$$\Delta V_{\text{victim}} = \frac{C_{\text{adj}}}{C_{\text{gnd-v}} + C_{\text{adj}}} \frac{1}{1+k} \Delta V_{\text{aggressor}}$$
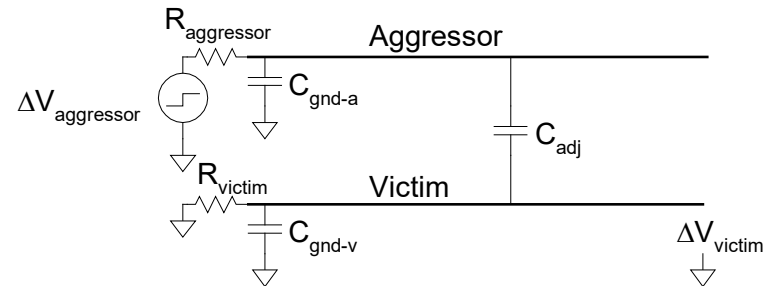
$$k = \frac{\tau_{\text{aggressor}}}{\tau_{\text{victim}}} = \frac{R_{\text{aggressor}} (C_{\text{gnd-a}} + C_{\text{adj}})}{R_{\text{victim}} (C_{\text{gnd-v}} + C_{\text{adj}})}$$


 
# Coupling Waveforms

- Simulated coupling for  $C_{\text{adj}} = C_{\text{victim}}$



# Noise Implications

- ❑ *So what* if we have noise?
- ❑ If the noise is less than the noise margin, nothing happens to digital circuits
- ❑ **Static CMOS logic** will eventually settle to correct output even if disturbed by large noise spikes
  - But glitches cause extra delay
  - Also cause extra power from false transitions
- ❑ **Dynamic logic** never recovers from glitches
- ❑ Memories and other sensitive circuits also can produce the wrong answer

# Wire Engineering

❑ Goal: achieve delay, area, power goals with acceptable noise

❑ Degrees of freedom:

- Width
- Spacing
- Layer
- Shielding

