


Combinational Circuits

Outline

- ☐ Input Ordering
- ☐ Symmetric Gates
- ☐ Asymmetric Gates
- ☐ Skewed Gates
- ☐ Circuit Families


Input Order

 - ❑ Our parasitic delay model was too simple to calculate parasitic delay for Y falling if
 - B arrives later than A?
 - A arrives later than B?




Input Order

 - Calculate parasitic delay for Y falling
 - If B arrives later?
 $t_{pdf} = R/2 * (2C) + (R/2 + R/2) * 6C = 7RC = 2.33\tau$
 - If A arrives later? $t_{pdf} = (R/2 + R/2) * 6C = 6RC = 2\tau$




Inner & Outer Inputs

 - ❑ **Outer** input is closest to rail (B) (V_{dd}/gnd rail)
- ❑ **Inner** input is closest to output (A)
- ❑ If input arrival time is known
 - Connect latest input to inner terminal




Symmetric Gates

 - Inputs can be made perfectly symmetric by connecting each input to inner and outer




Asymmetric Gates

 - ❑ Asymmetric gates **favor one input over another**
- ❑ Ex: suppose input A of a NAND gate is most critical
 - Use smaller transistor on A (less capacitance)
 - Boost size of noncritical input
 - So total resistance is same





 - ❑ $g_A =$
- ❑ $g_B =$
- ❑ $g_{\text{total}} = g_A + g_B =$
- ❑ Asymmetric gate approaches $g = 1$ on critical input
- ❑ But total logical effort goes up




Asymmetric Gates

- ❑ Asymmetric gates **favor one input over another**
- ❑ Ex: suppose input A of a NAND gate is most critical
 - Use smaller transistor on A (less capacitance)
 - Boost size of noncritical input
 - So total resistance is same
- ❑ $g_A = 10/9$
- ❑ $g_{\text{reset}} = 2$
- ❑ $g_{\text{total}} = g_A + g_{\text{reset}} = 28/9$
- ❑ Asymmetric gate approaches **$g = 1$ on critical input**
- ❑ But total logical effort goes up

  

Skewed Gates

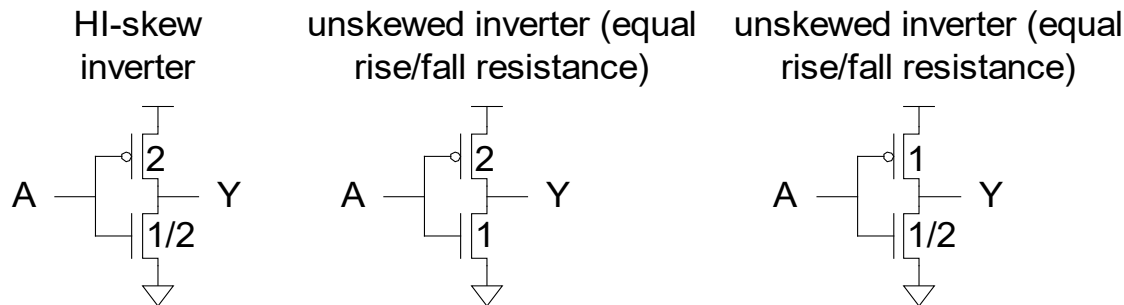
- ❑ Skewed gates favor **one edge over another**
- ❑ Ex: suppose rising output of inverter is most critical
 - Downsize noncritical nMOS transistor



- ❑ Calculate logical effort by comparing skewed gate to unskewed inverter with same effective resistance on **that edge**.
 - $g_u =$
 - $g_d =$

Skewed Gates

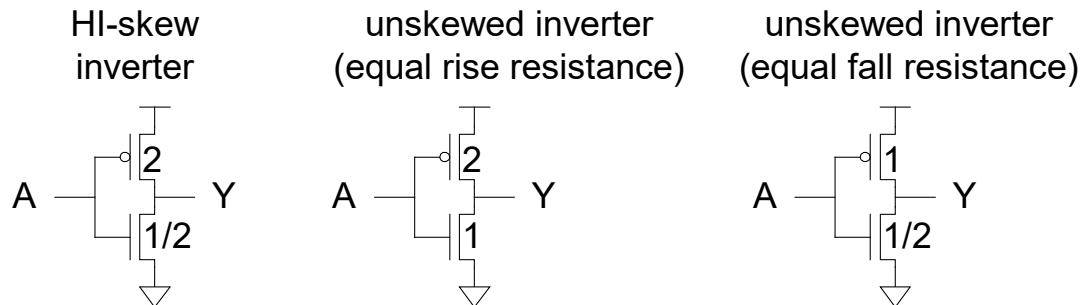- ❑ Skewed gates **favor one edge over another**
- ❑ Ex: suppose rising output of inverter is most critical
 - Downsize noncritical nMOS transistor



- ❑ Calculate logical effort by comparing skewed to unskewed inverter with same effective resistance on that edge.
 - $g_u = 2.5 / 3 = 5/6$ up logical effort
 - $g_d = 2.5 / 1.5 = 5/3$ down logical effort

HI- and LO-Skew Summary

- ❑ Def: Logical effort of a skewed gate for a particular transition is the ratio of the input capacitance of that gate to the input capacitance of an unskewed inverter delivering the same output current for the **same transition**.
- ❑ Skewed gates reduce size of noncritical transistors
 - HI-skew gates favor rising output (small nMOS)
 - LO-skew gates favor falling output (small pMOS)
- ❑ Logical effort is smaller for favored direction
- ❑ But larger for the other direction




Catalog of Skewed Gates

Inverter




NAND2

NOR2




unskewed

   

HI-skew

   

LO-skew

   




Catalog of Skewed Gates

Inverter




NAND2

NOR2




unskewed

   

HI-skew

   

LO-skew

   




Catalog of Skewed Gates

Inverter




NAND2

NOR2




unskewed

   

HI-skew

   


LO-skew

   



Circuit Families Introduction

 - ❑ What makes a circuit fast?
 - $I = C \, dV/dt \rightarrow t_{pd} \propto (C/I) \Delta V$
 - low capacitance
 - high current
 - small swing
- ❑ Logical effort is proportional to C/I
- ❑ pMOS are the enemy!
 - High capacitance for a given current
- ❑ Can we take the pMOS capacitance off the input?
- ❑ Various circuit families try to do this...




Pseudo-nMOS

  - ❑ In the old days, nMOS processes had no pMOS
 - Instead, use pull-up transistor that is always ON
- ❑ In CMOS, use a pMOS that is always ON
 - *Ratio* issue
 - Make pMOS about $\frac{1}{4}$ effective strength of pulldown network ($\frac{1}{3}$ — $\frac{1}{6}$)




Pseudo-nMOS Gates

 
- ❑ Design for unit current on output to compare with unit inverter.
- ❑ pMOS fights nMOS




Inverter

 

NAND2

 


NOR2

 


Pseudo-nMOS Gates

 
- ❑ Design for unit current on output to compare with unit inverter.
- ❑ pMOS fights nMOS




Inverter

 

NAND2

 


NOR2

 

Pseudo-nMOS Power

 - ❑ Pseudo-nMOS draws power whenever $Y = 0$
 - Called static power $P = I \cdot V_{DD}$
 - A few μA / gate * 1M gates would be a problem
- ❑ Use pseudo-nMOS sparingly for wide NORs
- ❑ Turn off pMOS when not in use



Ratio Example

- ❑ The chip contains a 32 word x 48 bit ROM
 - Uses pseudo-nMOS decoder and bitline pullups
 - On average, one wordline and 24 bitlines are high
- ❑ Find static power drawn by the ROM
 - $I_{\text{on-p}} = 36 \mu\text{A}$, $V_{DD} = 1.0 \text{ V}$





❑ Solution:

$$P_{\text{pull-up}} = V_{DD} I_{\text{pull-up}} = 36 \mu\text{W}$$

$$P_{\text{static}} = (31 + 24) P_{\text{pull-up}} = 1.98 \text{ mW}$$




Dynamic Logic

    - ❑ *Dynamic* gates uses a clocked pMOS pullup
- ❑ Two modes: *precharge* and *evaluate*




The Foot

   
- ❑ What if pulldown network is ON during precharge?
- ❑ Use series evaluation transistor to prevent fight.




Dynamic Logical Effort

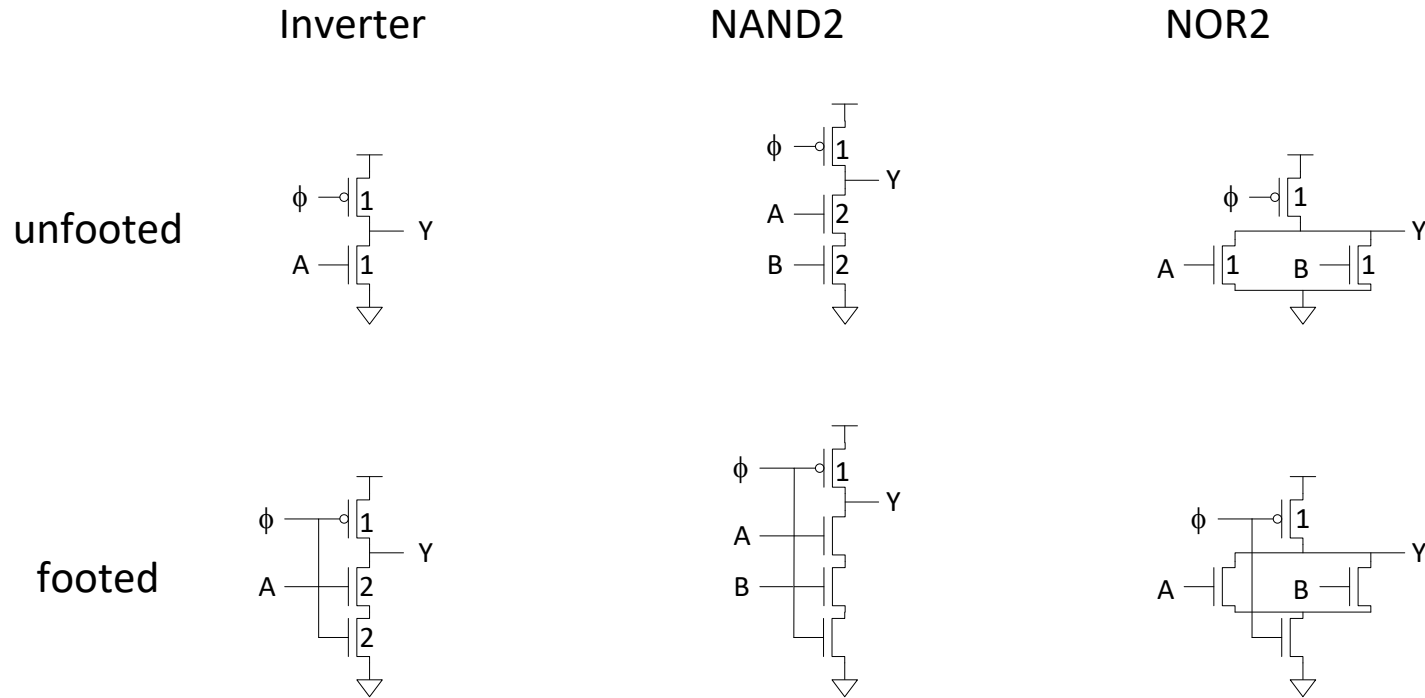

Dynamic Logical Effort

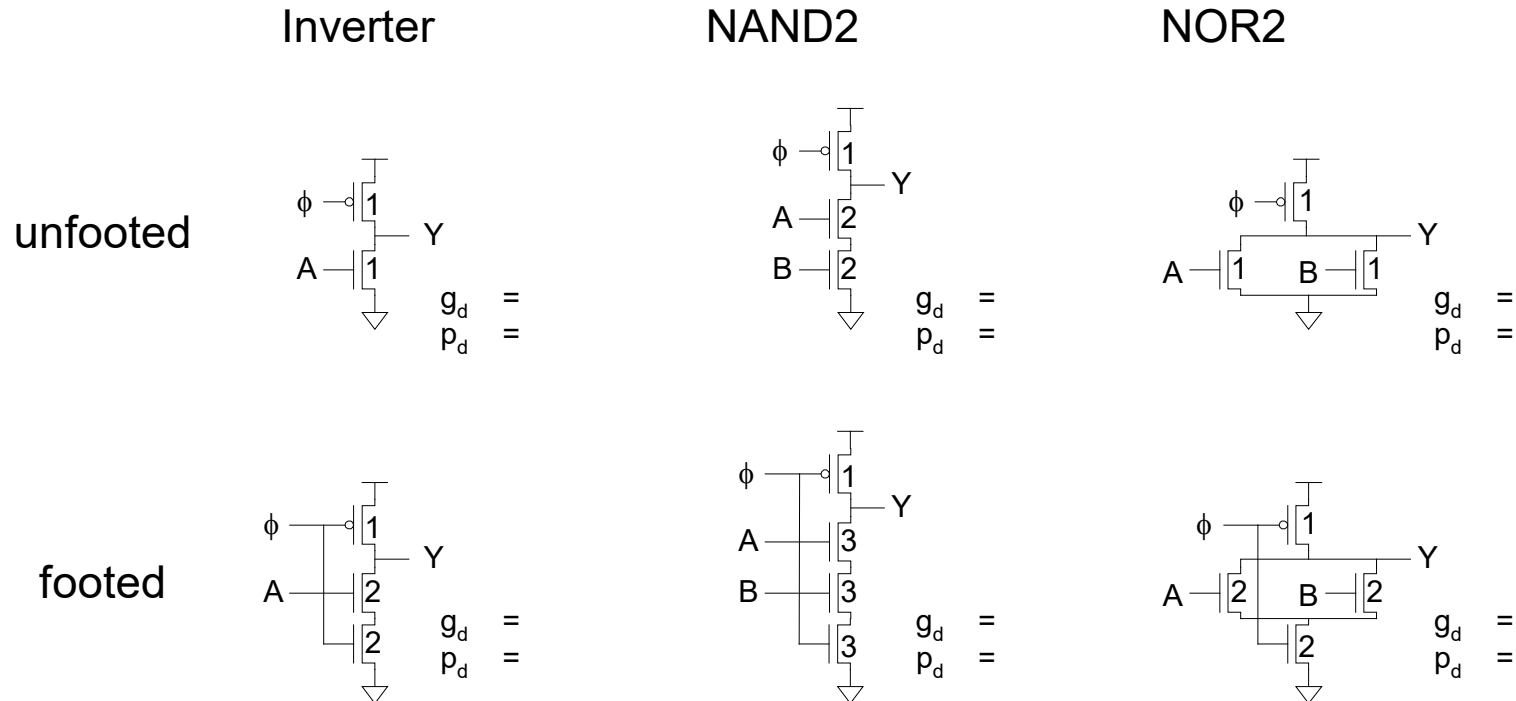


Dynamic Logical Effort

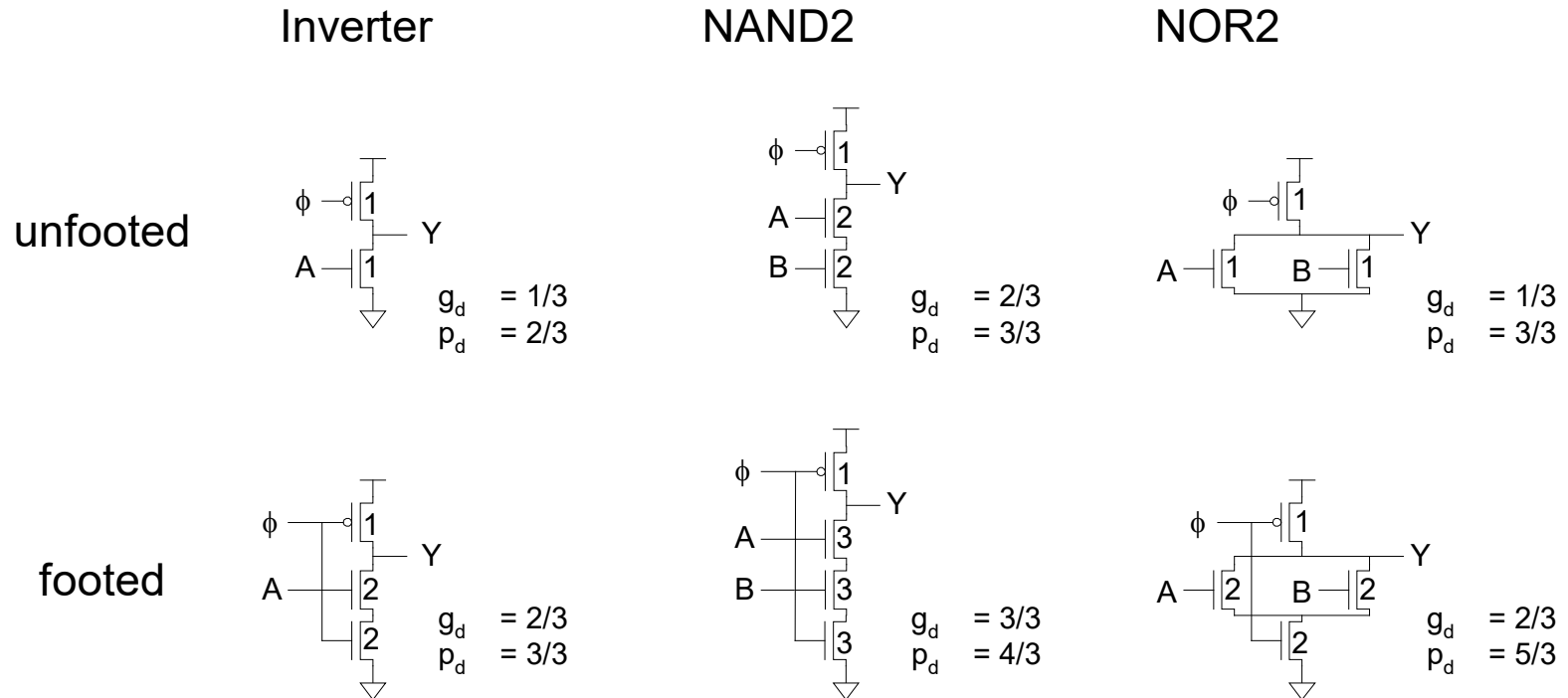

Monotonicity



- ❑ Dynamic gates require *monotonically rising* inputs during evaluation

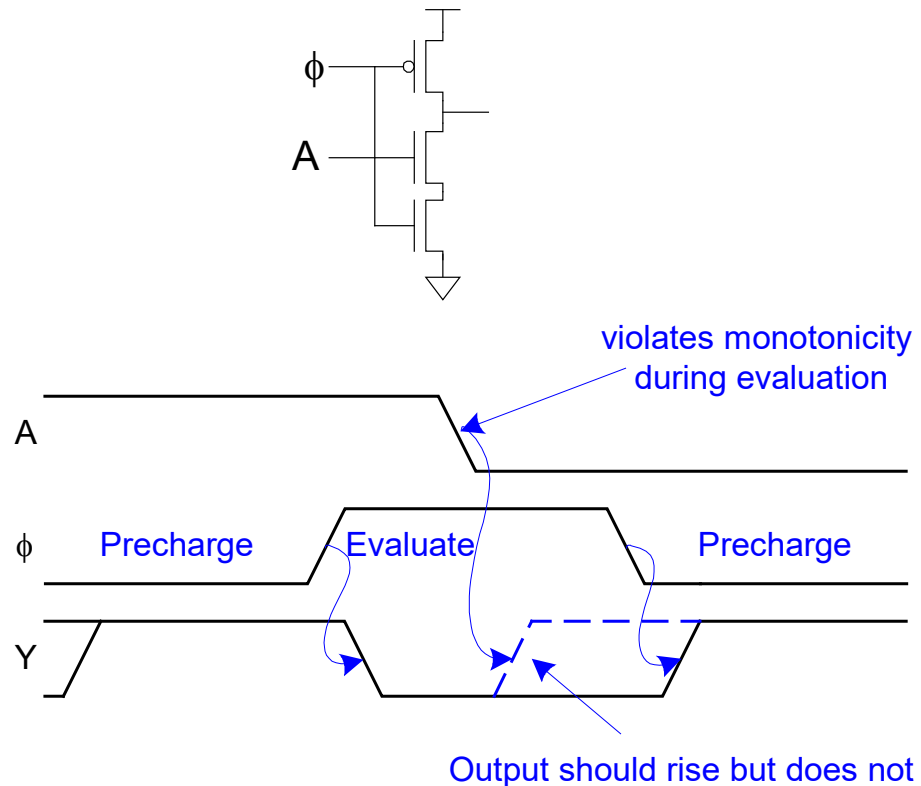- 0 \rightarrow 0
- 0 \rightarrow 1
- 1 \rightarrow 1
- But **not** 1 \rightarrow 0





Monotonicity Woes

  - ❑ But dynamic gates produce **monotonically falling outputs** during evaluation
- ❑ Illegal for one dynamic gate to drive another!



Monotonicity Woes

  - ❑ But dynamic gates produce monotonically falling outputs during evaluation
- ❑ Illegal for one dynamic gate to drive another!



Domino Gates

- ❑ Follow dynamic stage with inverting static gate
 - Dynamic / static pair is called **domino gate**
 - Produces monotonic outputs

