 


Logical Effort Outline

- ☐ Introduction
- ☐ Delay in a Logic Gate
- ☐ Multistage Logic Networks
- ☐ Choosing the Best Number of Stages
- ☐ Example
- ☐ Summary

Introduction

- ❑ Chip designers face a bewildering array of choices
 - (x) What is the best circuit topology for a function?
 - How many stages of logic give least delay?
 - How wide should the transistors be?
- ❑ Logical effort is a method to make these decisions
 - Uses a simple model of delay
 - Allows back-of-the-envelope calculations
 - Helps make rapid comparisons between alternatives
 - Emphasizes remarkable symmetries



Example


- ❑ Ben Bitdiddle is the memory designer for the Motorola 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.

- ❑ Decoder specifications:

- 16 word register file
- Each word is 32 bits wide
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs $A[3:0]$
- Each input may drive 10 unit-sized transistors

- ❑ Ben needs to decide:

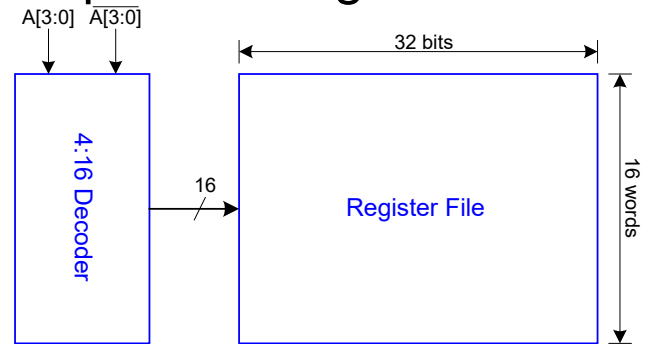- How many stages to use?
- How large should each gate be?
- How fast can decoder operate?



Delay in a Logic Gate

- Express (normalized) delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

$\tau = 3RC$ is the delay of an ideal fanout of 1 inverter with no parasitic capacitance

≈ 12 ps in 180 nm process

40 ps in 0.6 μm process

Delay in a Logic Gate (cont1)

- ❑ Express(normalized) delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- ❑ Delay has two components

$$d = f + p$$

- ❑ *Effort delay $f = gh$ (a.k.a. stage effort)*
 - Again f has two components

Delay in a Logic Gate (cont2)

- ❑ Express(normalized) delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- ❑ Delay has two components

$$d = f + p$$

- ❑ Effort delay $f = gh$ (also known as stage effort)
 - Again f has two components
 - g : *logical effort*
 - Measures relative ability of gate to deliver current
 - $g \equiv 1$ for inverter

Delay in a Logic Gate (cont3)

- ❑ Express(normalized) delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- ❑ Delay has two components

$$d = f + p$$

- ❑ Effort delay $f = gh$ (a.k.a. stage effort)

- g : logical effort
- h : electrical effort = C_{load} / C_{in}
 - Ratio of load capacitance to input capacitance
 - Sometimes called fanout

Delay in a Logic Gate (cont4)

- ❑ Express(normalized) delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- ❑ Delay has two components

$$d = f + p$$

- ❑ Parasitic delay p
 - Represents delay of gate driving itself (no load)
 - Set by internal parasitic capacitance (C_{db} , C_{sb})

Delay Plots


$$d = f + p = gh + p$$

As recalled, the rising delay of 2-input NAND gate with h fanout is

$$d_{abs} = (4h+6)RC$$


$$d = \frac{d_{abs}}{\tau} = \frac{(4h+6)RC}{3RC} = \left(\frac{4}{3}\right)h + 2$$

 - ☐ What about NOR2?
- ☐ What about (ab+c)?




Computing Logical Effort

 
- ❑ Def: *Logical effort is the ratio of **input** capacitance of the analyzed **gate** to **input** capacitance of **an inverter** delivering the same output current (same effective resistance).*
- ❑ Measure from delay vs. fanout plots; g =slope
- ❑ Or estimate by counting transistor widths



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 4$$
$$g = 4/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$

Catalog of Gates

- Logical effort (g) of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		$4/3$	$5/3$	$6/3$	$(n+2)/3$
NOR		$5/3$	$7/3$	$9/3$	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	


Catalog of Gates

- ❑ Parasitic delay of common gates
 - In multiples of p_{inv} (≈ 1)

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

 Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g =$

Electrical Effort: $h =$


Parasitic Delay: $p =$

Stage Delay: $d =$

Frequency: $f_{\text{osc}} =$

 Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g = 1$

Electrical Effort: $h = 1$

Parasitic Delay: $p = 1$


Stage Delay: $d = 2$

Frequency: $f_{\text{osc}} = 1/(2 \cdot N \cdot d) = 1/(4N)$

31 stage ring oscillator in
0.6 μm process has
frequency of ~ 200 MHz

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g =$


Electrical Effort: $h =$

Parasitic Delay: $p =$

Stage Delay: $d =$

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g = 1$

Electrical Effort: $h = 4$

Parasitic Delay: $p = 1$

Stage Delay: $d = 5$

The FO4 delay is about

200 ps in 0.6 μm process

60 ps in a 180 nm process

$f(1/3 - 1/2)$ ps in an f nm process


Multistage Logic Networks

❑ Logical effort generalizes to multistage networks

❑ *Path Logical Effort* $G = \prod g_i$

❑ *Path Electrical Effort* $H = \frac{C_{load-path}}{C_{in-path}}$

 ❑ *Path Effort* $F = \prod f_i = \prod g_i h_i$



Multistage Logic Networks

- ❑ Logical effort generalizes to multistage networks

- ❑ *Path Logical Effort* $G = \prod g_i$

- ❑ *Path Electrical Effort* $H = \frac{C_{load-path}}{C_{in-path}}$

- ❑ *Path Effort* $F = \prod f_i = \prod g_i h_i$

- ❑ Can we write $F = GH$?

Paths that Branch

❑ No! Consider paths that branch:

G =


H =

GH =

h_1 =

h_2 =

F = GH?

 

Paths that Branch

❑ No! Consider paths that branch:

$$G = 1(1) = 1$$


$$H = 90 / 5 = 18$$

$$GH = 18$$

$$h_1 = (15 + 15) / 5 = 6$$

$$h_2 = 90 / 15 = 6$$

$$F = g_1 h_1 g_2 h_2 = 36 = 2GH$$

 

Branching Effort

- ❑ Introduce *branching effort*
 - Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- ❑ Now we compute the path effort
 - $F = GBH$

Multistage Delays

- ❑ Path Effort Delay $D_F = \sum f_i$
- ❑ Path Parasitic Delay $P = \sum p_i$
- ❑ Path Delay $D = \sum d_i = D_F + P$

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is the smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}} \quad \text{best stage effort}$$

- Thus minimum delay of N stage path is

$$D = NF^{\frac{1}{N}} + P$$

- This is a **key** result of logical effort
 - Find smallest possible delay
 - Doesn't require calculating gate sizes

Gate Sizes

- How wide should the gates be for least delay?


$$\hat{f} = gh = f_i = g_i \frac{C_{load}(i)}{C_{in}(i)}$$

$$\Rightarrow C_{in}(i) = \frac{g_i C_{load}(i)}{\hat{f}}$$

- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.

 
Example: 3-stage path

- Select gate sizes x and y for least delay from A to B



Delay $D =$

Example: 3-stage path

 

Logical Effort

$$G = (4/3) * (5/3) * (5/3) = 100/27$$

Electrical Effort

$$H = 45/8$$

Branching Effort

$$B = 3 * 2 = 6$$

Path Effort

$$F = GBH = 125$$

Best Stage Effort

$$\hat{f} = \sqrt[3]{F} = 5$$

Parasitic Delay

$$P = 2 + 3 + 2 = 7$$

Delay

$$D = 3 * 5 + 7 = 22 = 4.4 \text{ FO4}$$


Example: 3-stage path

- Work backward for sizes

$$Cin_i = (W_p + W_n) = \frac{g_i C_{load_i}}{f}$$

y =

x =

 


Example: 3-stage path

- Work backward for sizes

$$y = (5/3) * 45 / 5 = 15$$

$$x = (5/3) * (15 * 2) / 5 = 10$$
 
$$Cin_i = (W_p + W_n)C = \frac{g_i C_{load i}}{\hat{f}}$$




Example: 3-stage path

- Work backward for sizes

$$y = 45 * (5/3) / 5 = 15$$

$$x = (15 * 2) * (5/3) / 5 = 10$$
 
$$Cin_i = (W_p + W_n) = \frac{g_i C_{load i}}{\hat{f}}$$




Best Number of Stages

- ❑ How many stages should a path use?
 - Minimizing number of stages is not always fastest
- ❑ Example: drive 64-bit data path with unit inverter

❑ $G=1$

$$H = \frac{64}{1} = 64$$

$$F = GBH = 64$$

 

Best Number of Stages


- ❑ How many stages should a path use?
 - Minimizing number of stages is not always fastest
- ❑ Example: drive 64-bit datapath with unit inverter

$F=64$

Best stage effort: $\hat{f} = F^{1/N}$

$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

 

Best Number of Stages


- ❑ How many stages should a path use?
 - Minimizing number of stages is not always fastest
- ❑ Example: drive 64-bit datapath with unit inverter

$$F=64$$

$$\text{Best stage effort: } \hat{f} = F^{1/N}$$

$$D = NF^{1/N} + P$$


$$= N(64)^{1/N} + N$$

 

Derivation

- Consider adding inverters to end of path
 - How many give least delay?
 
$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$



$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

- Define best stage effort $\rho = F^{\frac{1}{N}}$

$$p_{inv} + \rho(1 - \ln \rho) = 0$$


Best Stage Effort

- ❑ $p_{inv} + \rho(1 - \ln \rho) = 0$ has no closed-form solution
- ❑ For $p_{inv} = 1$, solve numerically for $\rho = 3.59$
- ❑ A path achieves the least delay by using the number of stages

$$\hat{N} = \log_{\rho} F$$

Sensitivity Analysis

 - How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$ gives delay within 15% of optimal
 - $\rho = 4$ is a reasonable number

Example, Revisited


- ❑ Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.

- ❑ Decoder specifications:

- 16 word register file
- Each word is 32 bits wide
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs $A[3:0]$
- Each input may drive 10 unit-sized transistors

- ❑ Ben needs to decide:

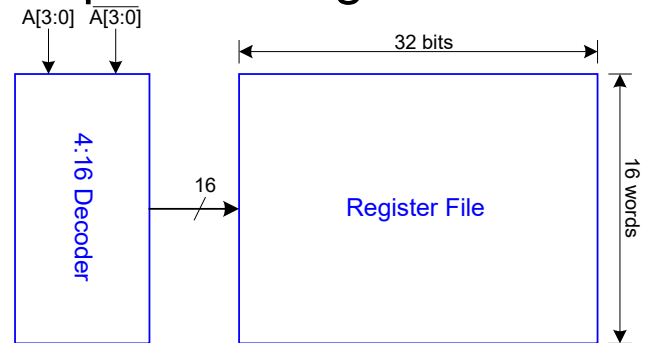- How many stages to use?
- How large should each gate be?
- How fast can decoder operate?



Number of Stages

- ❑ Decoder effort is mainly electrical and branching

Electrical Effort: $H = (32 \cdot 3) / 10 = 9.6$

Branching Effort: $B = 16/2 = 8$

- 16 bit decoder will be wired to either the address (A3-A0) or the address not (A3'-A0'), two options.

- ❑ If we neglect logical effort (assume $G = 1$)

Path Effort: $F = GBH = 76.8$

Number of Stages: $N = \log_4 F = 3.1$

- ❑ Try a 3-stage design

Gate Sizes & Delay

Logical Effort: $G =$


Path Effort: $F =$

Stage Effort: $\hat{f} =$

Path Delay: $D =$

Gate sizes: $z =$

$y =$

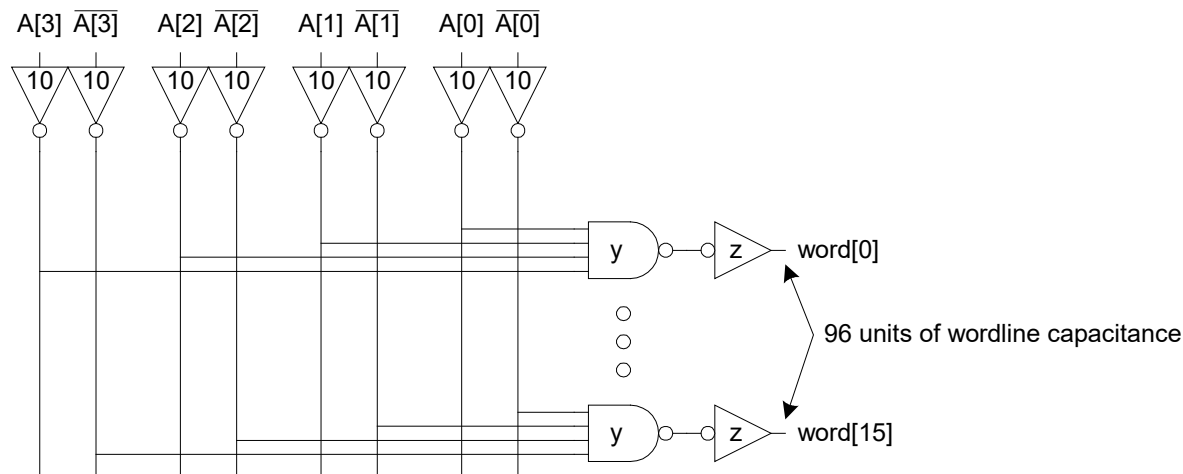

Gate Sizes & Delay


Logical Effort: $G = 1 * 6/3 * 1 = 2$

Path Effort: $F = GBH = 2 \cdot 8 \cdot 9.6 = 154$

Stage Effort: $\hat{f} = F^{1/3} = 5.36$

Path Delay: $D = 3\hat{f} + 1 + 4 + 1 = 22.1$

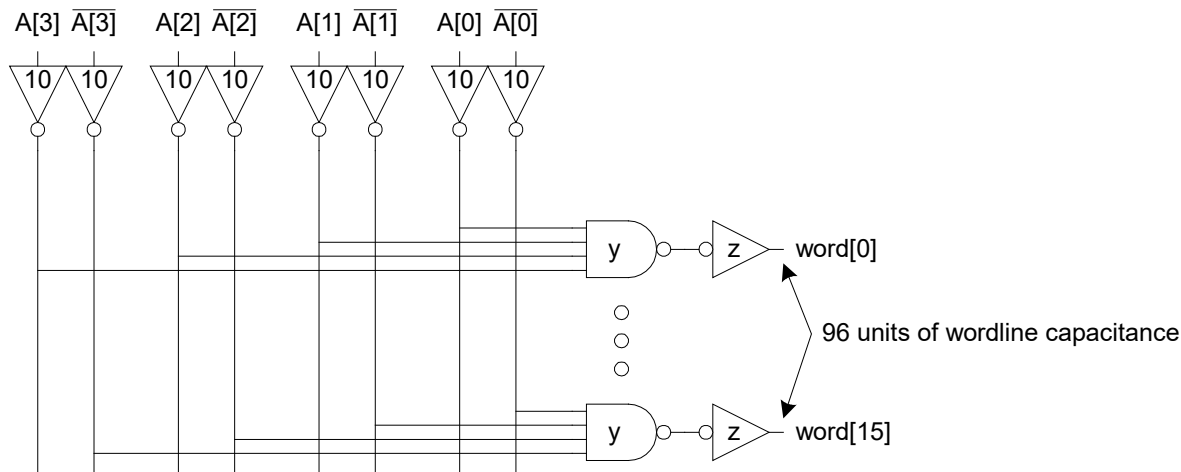Gate sizes: $z = 96^{1/5.36} = 18$ $y = 18^{2/5.36} = 6.7$



Comparison

- ❑ Compare many alternatives with a spreadsheet

Design	N	G	P	D
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

Review of Definitions

Term	Stage	Path
number of stages	1	N
logical effort	g	$G = \prod g_i$
electrical effort	$h = \frac{C_{load}}{C_{in}}$	$H = \frac{C_{load-path}}{C_{in-path}}$
branching effort	$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH = \prod f_i$
effort delay	f	$D_F = \sum f_i$
parasitic delay	p	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

Method of Logical Effort

1) Compute path effort

$$F = GBH$$

2) Estimate best number of stages

$$N = \log_4 F$$

3) Sketch path with N stages

4) Estimate least delay

$$D = NF^{\frac{1}{N}} + P$$

5) Determine best stage effort

$$\hat{f} = F^{\frac{1}{N}}$$

6) Find gate sizes $C_{in_i} = \frac{g_i C_{Li}}{\hat{f}}$

7) Using rising effective resistance equals falling effective resistance to find N and P transistors sizes

Limits of Logical Effort

- ❑ Linear delay model fails to capture the effort of input slope
- ❑ Logical Effort does not account for Interconnect
 - Iteration required in designs with wire
- ❑ Logical effort is most applicable to high speed circuit with regular layouts where routing delay does not dominate
- ❑ Maximum speed only
 - Not minimum area/power for constrained delay
- ❑ Paths with complex branching are difficult to analyze by hand.

Summary

- ❑ Logical effort is useful for thinking of delay in circuits
 - Numeric logical effort characterizes gates
 - NANDs are faster than NORs in CMOS
 - Paths are fastest when stage effort is ~ 4
 - Path delay is *weakly sensitive to stages, sizes*
 - But using fewer stages doesn't mean faster paths
 - Delay of path is about $\log_4 F$, FO4 inverter delays
 - Inverters and NAND2 best for driving large caps
 - Practical limit of about *4 transistors in series and 4 inputs to multiplexers*
- ❑ Provides language for discussing fast circuits

HW

❑ 4.3, 4.4, 4.6, 4.9, 4.10, 4.11