
Under content/HW in your pilot, there are some home exercise questions along with their brief answers for you to practice.

Circuit Outline

- ☐ CMOS Gate Design
- ☐ Pass Transistors
- ☐ Transmission gate
- ☐ Tristate
- ☐ Multiplexer
- ☐ CMOS Latches & Flip-Flops


CMOS Gate Design

- ❑ Activity:
 - Sketch a 4-input CMOS NOR gate

Series and Parallel


- ❑ nMOS: 1 = ON
- ❑ pMOS: 0 = ON
- ❑ *Series*: all must be ON

- ❑ *Parallel*: any can be ON

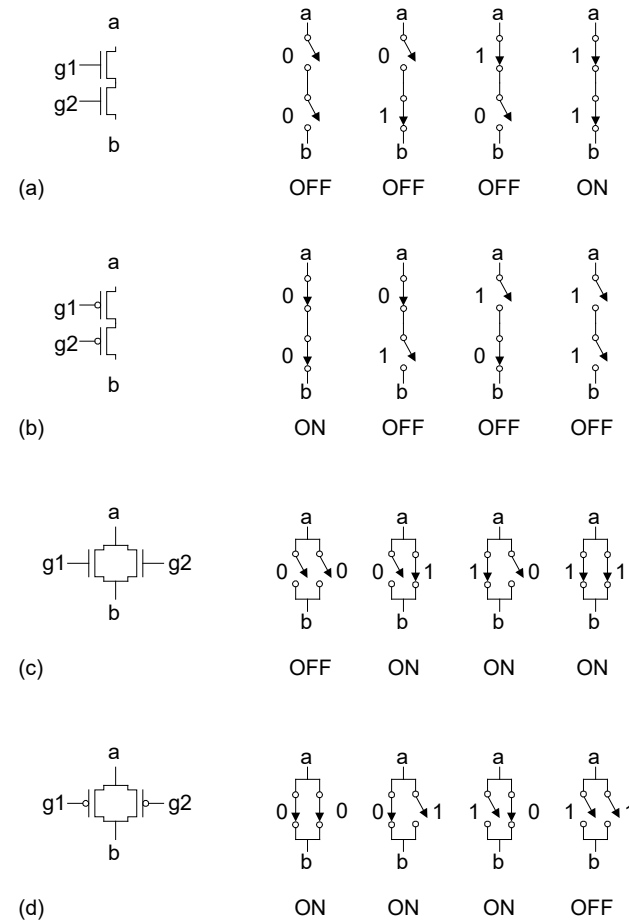

Conduction Complement

 - ❑ Complementary CMOS gates always produce 0 or 1 for digital circuits
- ❑ Ex: NAND gate
 - Series nMOS: $Y=0$ when both inputs are 1
 - Thus $Y=1$ when either input is 0
 - Requires parallel pMOS
- ❑ Rule of *Conduction Complements*
 - Pull-up network is complement of pull-down
 - Parallel \rightarrow series, series \rightarrow parallel



Compound Gates—inverting circuit

Ex: $Y = \overline{(A \cdot B) + (C \cdot D)}$ —this function is sometimes called AND-OR-INVERT-22 or AOI22 because it performs the NOR of a pair of 2-input ANDs

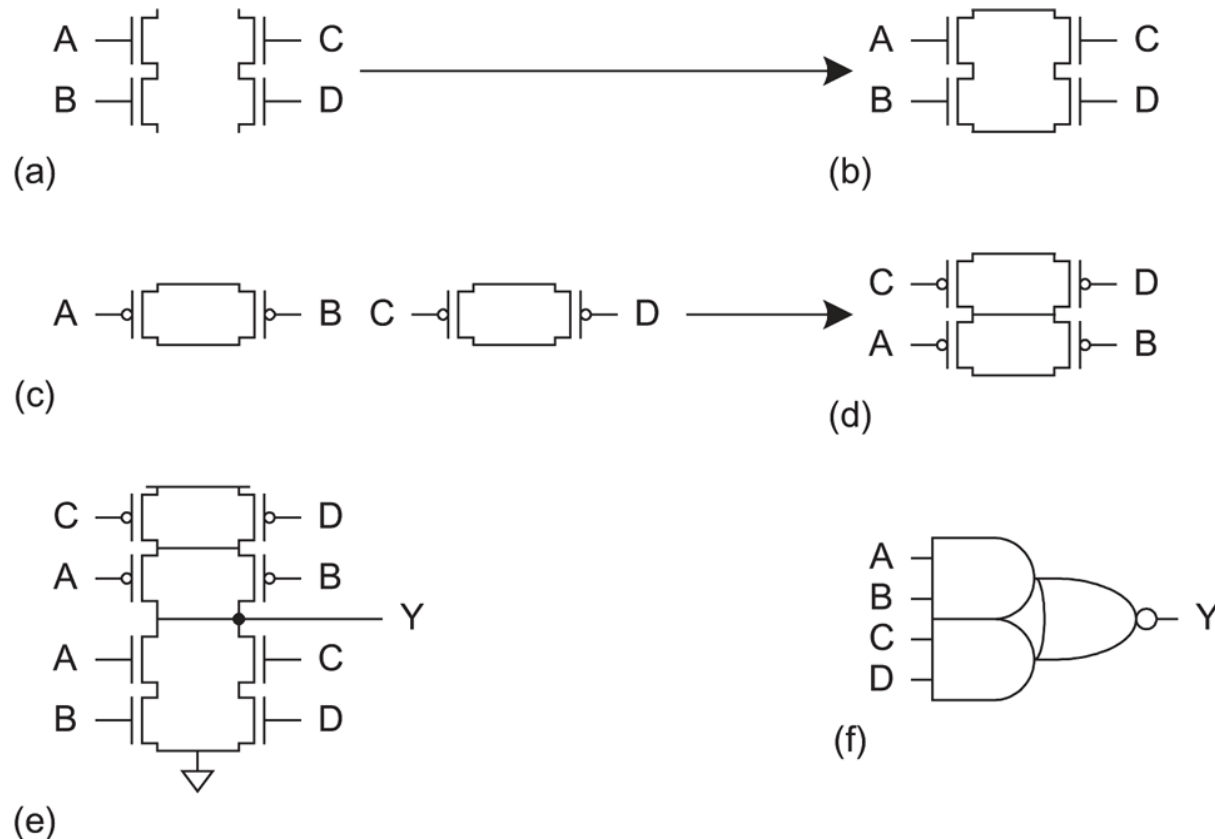


FIG 1.17 CMOS compound gate for function $Y = \overline{(A \cdot B) + (C \cdot D)}$

$Z = \overline{(abc + d)}$ is called AOI31; $Z = \overline{(ab + cd + e)}$ is called AOI221

Non-inverting circuits

- ❑ In general, the circuit outputs are not always the inverted inputs function
- ❑ Example 1 $F=abc$
 - Two ways
 1. Straight forward--adding an inverter to output
let $G=\overline{(abc)}$, $F=G=\overline{(abc)}$
Total transistors = $6+2=8$
 2. Double inverter and use De Morgan—
 $\overline{\overline{F}}=\overline{\overline{(abc)}}=\overline{\overline{a} + \overline{b} + \overline{c}} \Rightarrow$
Which required three inverters
Total transistors = $6+6=12$

Non-inverting circuits (Cont)

□ Example 2

$$Z = (A+B)\bar{C}\bar{D} = \bar{Z} + D$$

A. Find ckt for $G = \bar{Z}$ and invert the output
transistors

14

B. Double inverter and use De Morgan (no output inverter)
transistors

$$Z = \overline{(a+b) + \bar{c} + \bar{d}} = \bar{a}\bar{b} + c + d$$

12

Non-inverting circuits (Cont)

❑ Example 3 $F=(a'+b')(c+d)$

A. Add inverter to output of G

$$F=G'; G'=\overline{((a'+b')(c+d))}$$

8+4+2=14 transistors

B. De Morgan (no inverter output)

$$F'=((a'+b')(c+d))'=(a'+b')'+(c+d)'$$

$$=ab+(c+d)'=ab+c'd'$$

8+4=12 transistors

❑ Which is a better design

❑ Exercise for yourself










1. Design both schematic and stick diagram for OR2/XOR2/NOR2/AND2 gates by using minimum CMOS transistors.
2. Design schematic CMOS compound gates for functions $Z=((a+b)(c+d))'$ and $Z=(a'b'c+d)$ using least number of transistors.

Signal Strength

- ❑ *Strength* of signal
 - How close the signal approximates to ideal voltage source
- ❑ V_{DD} and GND rails are strongest '1' and '0'
- ❑ nMOS passes strong '0'
 - But degraded or weak '1'
- ❑ pMOS passes strong '1'
 - But degraded or weak '0'
- ❑ Thus nMOS are best for pull-down network and pMOS are best for pull-up network


Pass Transistors

- Transistors can be used as switches

         

Pass Transistors

 - ❑ We have assumed source is grounded
- ❑ What if source > 0 ?
 - e.g. pass transistor passing V_{DD}




Pass Transistors

- ❑ We have assumed source is grounded

- ❑ What if source > 0 ?

 - e.g. pass transistor passing V_{DD}

 

- ❑ $V_g = V_{DD}$

 - If $V_s > V_{DD} - V_t$, $V_{gs} < V_t$

 - Hence transistor would turn itself off





- ❑ nMOS pass transistors pull no higher than $V_{DD} - V_{tn}$

 - Called a degraded “1”





 - Approach degraded value slowly (low I_{ds})

- ❑ pMOS pass transistors pull no lower than $|V_{tp}|$

Pass Transistor Ckts

    


Pass Transistor Ckts

    


Transmission Gates

 
- ❑ Pass transistors produce degraded outputs
- ❑ *Transmission gates* pass both 0 and 1 well



$g = 0, gb = 1$

 


$g = 1, gb = 0$

 





Input

Output

$g = 1, gb = 0$

 



$g = 1, gb = 0$

    

Tristates


- ❑ *Tristate buffer* produces Z when not enabled

EN	A	Y
0	0	
0	1	
1	0	
1	1	

  


Nonrestoring Tristate

 - ❑ Transmission gate acts as tristate buffer
 - Only two transistors
 - But *nonrestoring*
 - Noise on A is passed on to Y



Tristate Inverter

 
- ❑ Tristate inverter produces restored output
 - Violates conduction complement rule
 - Because we want a Z output



Multiplexers

- ❑ 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	
0	X	1	
1	0	X	
1	1	X	

 


Gate-Level Mux Design

- ❑ $Y = SD_1 + \bar{S}D_0$ (too many transistors)
- ❑ How many transistors are needed?


Transmission Gate Mux

 - ❑ Nonrestoring mux uses two transmission gates
 - Only 6 transistors





Inverting Mux

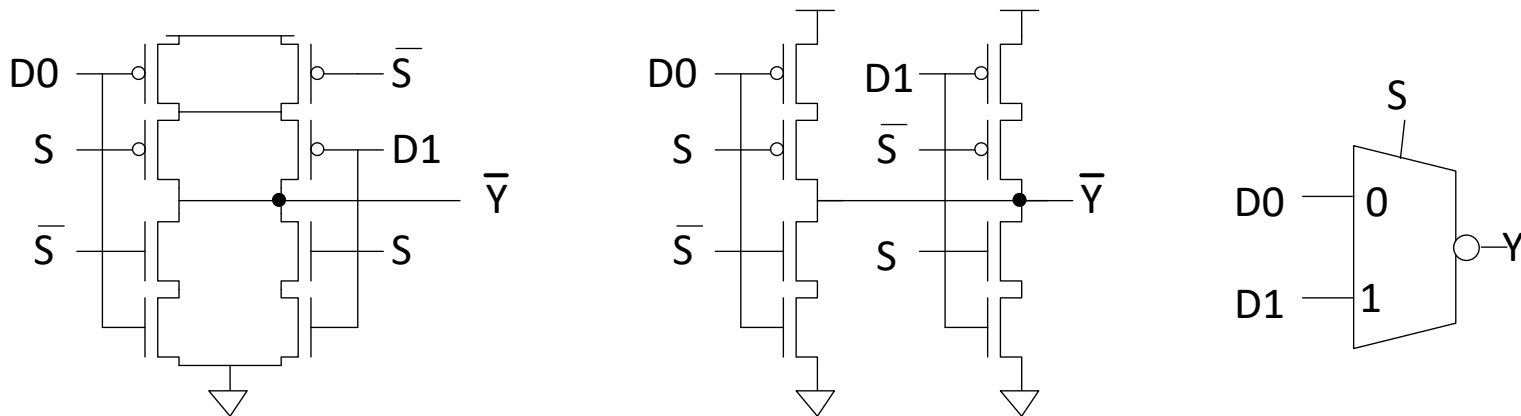- ❑ Inverting multiplexer
 - Use compound AOI22
 - Or pair of tristate inverters
 - Essentially the same thing
- ❑ Noninverting multiplexer adds an inverter



  
4:1 Multiplexer

- ❑ 4:1 mux chooses one of 4 inputs using two selects
 - Two levels of 2:1 muxes
 - Or four tristates





D Latch

 - ❑ When **CLK = '1'**, latch is *transparent*
 - D flows through to Q like a buffer
- ❑ When CLK = '0', the latch is *opaque*
 - Q holds its old value independent of D
- ❑ a.k.a. *transparent latch* or *level-sensitive latch*







D Latch Design

- ❑ Multiplexer chooses D or old Q

  


D Latch Operation

    


D Flip-flop

 - ❑ When CLK **rises**, D is copied to Q
- ❑ At all other times, Q holds its value
- ❑ a.k.a. *positive edge-triggered flip-flop*, *master-slave flip-flop*



D Flip-flop Design

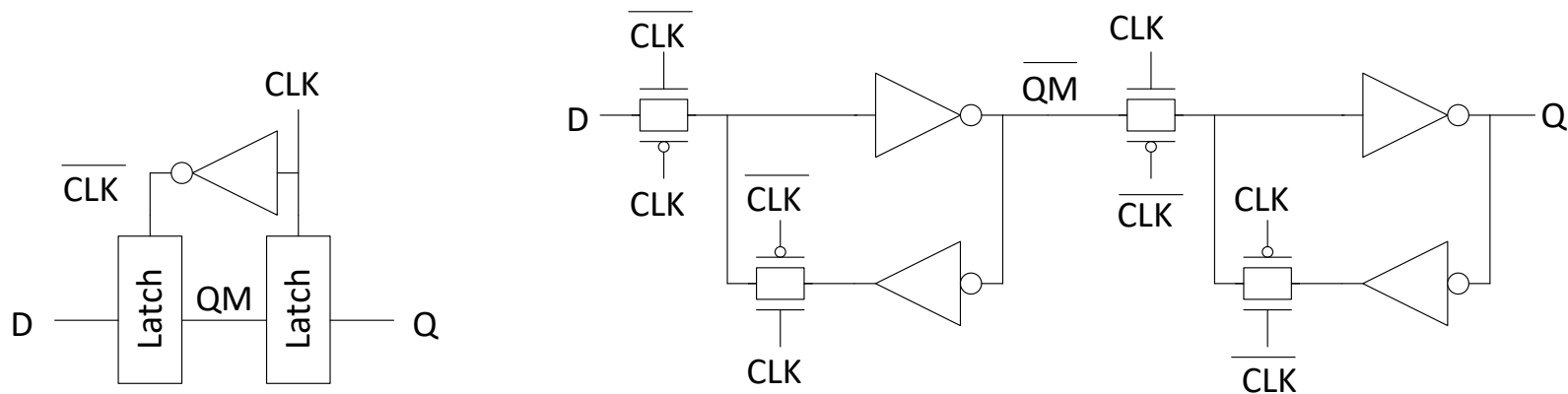- ❑ Built from master and slave D latches



D Flip-flop Operation

